

UART

Introduction:

UART is a protocol that can be applied to any transmitter and receiver for data communication.

Universal - The protocol can work with any compatible transmitter and receiver.

Asynchronous - No clock signal is used for data communication. Instead, the devices agree on a data rate in advance and synchronize only during the start and stop bits of each data frame.

When two devices communicate using UART, they need at least two connections between them: one for transmission (TX) and one for reception (RX).

UART is a character-oriented protocol, meaning data is sent byte by byte. Each communication uses a specific bit frame structure, including start bits, data bits, optional parity bits, and stop bits. This bit frame structure allows consistent data exchange between devices.


Serial Communication and parallel Communication:

Parallel communication:

- High Speed Communication
- Generally, Processor modules communicating in parallel

Serial communication:

 - Low speed communication
- Long distance communication, like computer to other peripherals



Limitations of parallel communication & Advantage of Serial communication

Generally, computer process the data in parallel and speed of the communication is high.



Limitation of Parallel:

- When we want transfer the data for a longer distance (> 1 feet)
- There may be difference in reaching of bits to the other end due to difference in thickness of the wire of that parallel lines

- Difference can be recognized when speed of operation (clock speed) is more
- So, there is chance to getting errors

Then what you do?

  - There is need to convert parallel → serial
- after transferring for a distance
- at receiver, convert serial → Parallel




Synchronous & Asynchronous Serial Communication:

Synchronous:


- Transfer Operation takes place using clock signal
- Neg-edge of clock, Transmits data from sender and next pos-edge of clock, Receives data at receiver

Asynchronous:

 - No Clock
- START BIT(0), STOP BIT(1)
- Data is provided between these two




Synchronous Transmission

 

Asynchronous Transmission

UART TOP Block Diagram:

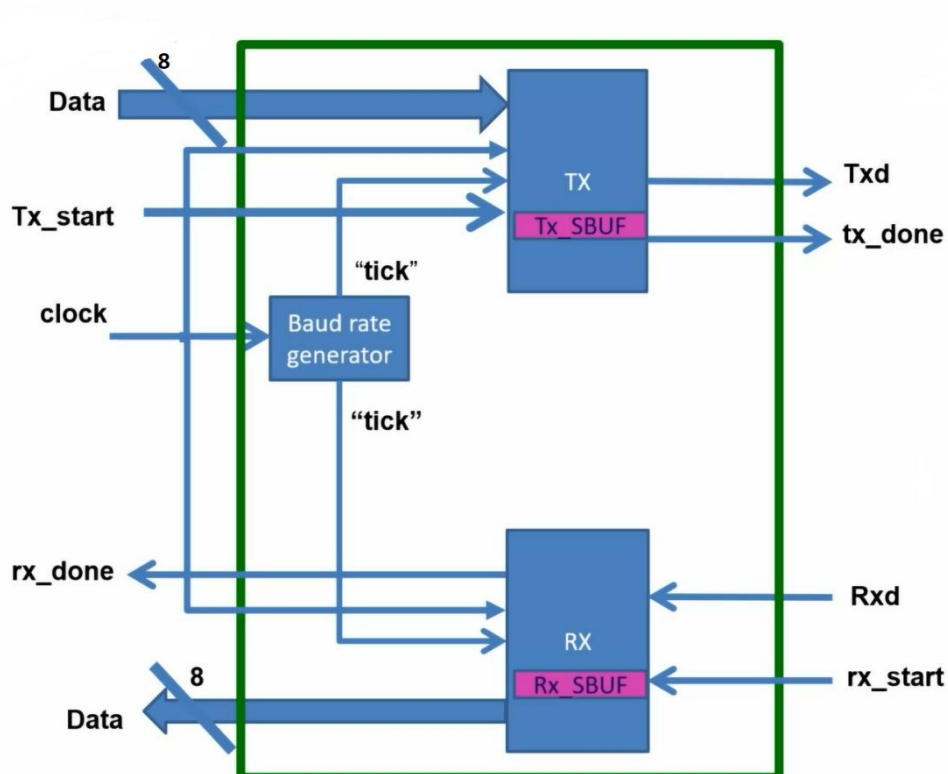

What is an UART:

Universal Asynchronous Receiver Transmitter

UART is an Integrated Circuit (IC)


It USES to converts

parallel data \longleftrightarrow Serial Data


SBUF is a Serial Buffer, is a shift register

Parallel \longrightarrow Serial: Shifting & transmits

 Serial \longrightarrow Parallel: Receiving & shifting



Frame format of UART:

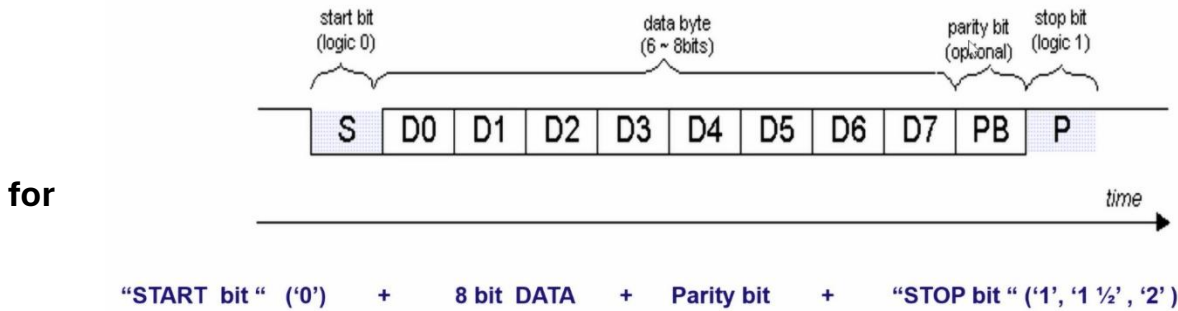

Buad rate generator UART:

Baud rate defined as bits/sec,

generally, baud rates are like 4800, 9600, 19200.

Let clock signal $\text{clk} = 50 \text{ MHz} = 50 \times 10^6$

Let us say we required baud rate of data in UART is 19200

So, based on our requirements, pulses will be generated at every = $(50 \times 10^6) / (19200) = 2604$


So, we need to design a counter Modulo-2605, i.e., counter counts (0-to-2604)

At every count value = 2604, one pulse need to generate, named as "tick" signal

At every "tick" signal, data need to send or receive.

Transmission and Reception:

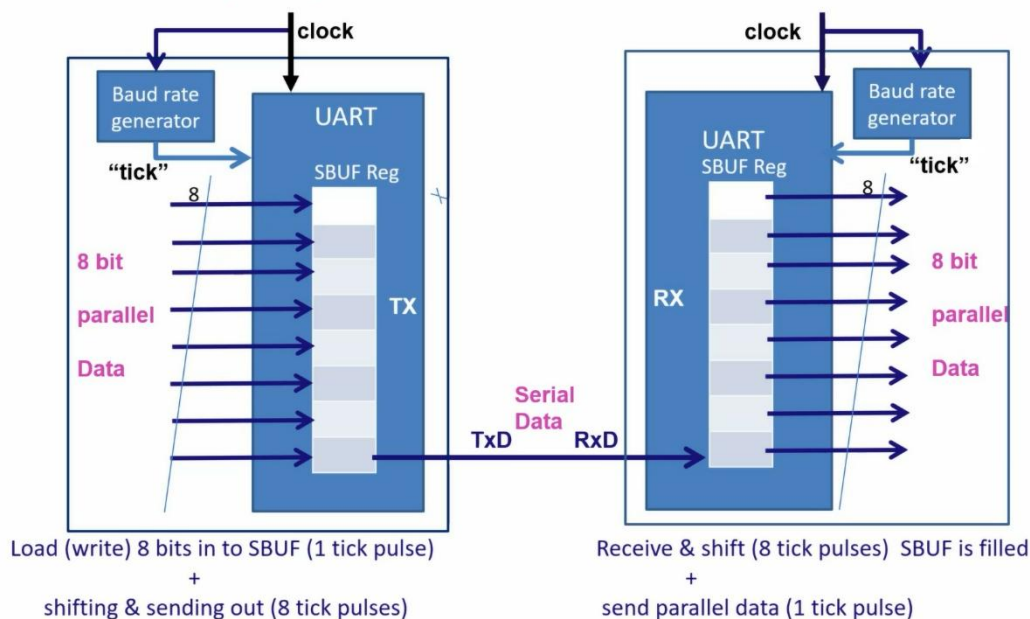Transmission & Reception Operation of UART



Data Transmission:

1. Parallel Data Input:

- The transmitting UART receives **8-bit parallel data** from a source (e.g., a microcontroller or processor).
- This data is loaded into the **Serial Buffer Register (SBUF)** in one tick pulse.

2. Data Conversion:

- The parallel data is shifted out **bit by bit** in synchronization with the **baud rate generator**.
- The baud rate generator provides clock pulses ("ticks") to control data shifting and transmission speed.

3. Serial Transmission:

- The bits are sent serially through the **TxD (Transmit Data) line**.
- The complete 8-bit data transmission requires **8 tick pulses**.
- The data is transmitted with start and stop bits (not shown in the diagram but essential in UART communication).

Data Reception:

1. Serial Data Reception:

- The receiving UART captures the incoming serial data stream from the **RxD (Receive Data) line**.
- The data is shifted into the **SBUF Register** bit by bit over **8 tick pulses**.


2. Parallel Conversion:

- Once all 8 bits are received, the data is converted from serial to parallel format.
- The complete **8-bit parallel data** is made available for processing in **1 tick pulse**.


3. Data Output:

- The received parallel data is then forwarded to the connected system for further processing.

Transmission FSM:

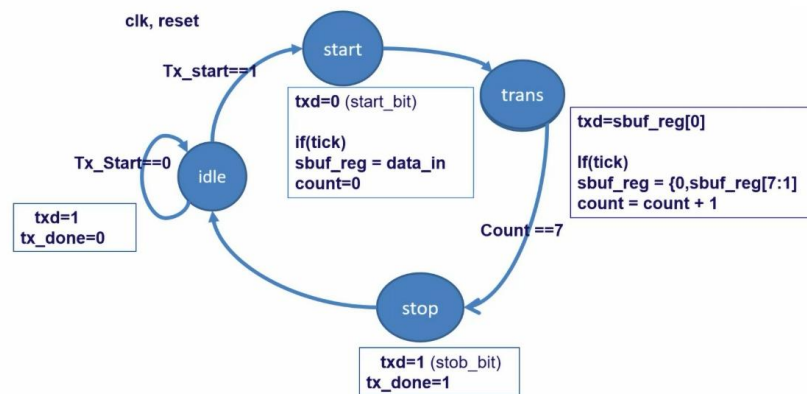

Reception FSM:

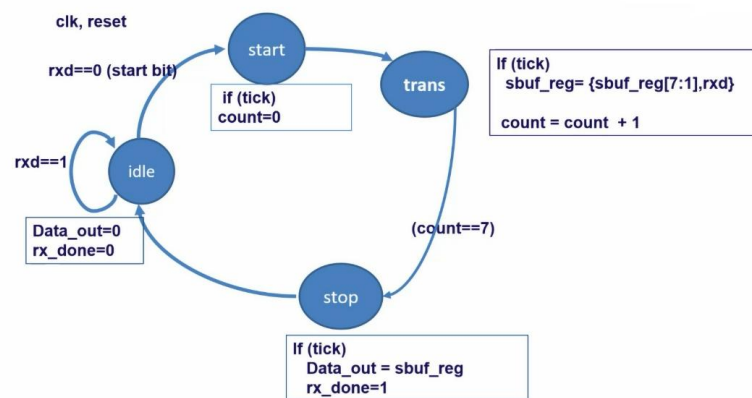

NOTE:

To understand the concept of UART practically, it is important to note that even though the **transmitter (TX module)**, **receiver (RX module)**, and **baud rate generator** exist within a single UART chip, actual data transfer occurs between two separate UARTs. The **TX module of one UART** transmits data to the **RX module of another UART**.

For **simulation (verification)**, it is not possible to test both transmission and reception using a single top module. A **top module is required only for synthesis** (i.e., hardware implementation).

If you want to **simulate both transmission and reception**, you need to use **two UARTs**—one UART's **TX module** will send data to the second UART's **RX module**. This introduces several **synchronization challenges** that need to be resolved. Such testing is typically performed at the **block level verification** stage rather than at the **system level**.